

CSE 331 - Spring 2021

Homework 3 Report

Coşkun Hasan ŞALTU
1801042631

1. Explanation of Moduls and Project

and4:This module gets two 4-bit input and give the answer of and operation of two input.

and32:This module gets two 32-bit input and give the answer of and operation of two input.This module use **and4** module 8 times.

or4:This module gets two 4-bit input and give the answer of or operation of two input.

or32:This module gets two 32-bit input and give the answer of or operation of two input.This module use **or4** module 8 times.

xor4:This module gets two 4-bit input and give the answer of xor operation of two input.

xor32:This module gets two 32-bit input and give the answer of xor operation of two input.This module use **xor4** module 8 times.

nor4:This module gets two 4-bit input and give the answer of nor operation of two input.

nor32:This module gets two 32-bit input and give the answer of nor operation of two input.This module use **nor4** module 8 times.

not4:This module gets two 4-bit input and give the answer of not operation of two input.

not32:This module gets two 32-bit input and give the answer of not operation of two input.This module use **not4** module 8 times.

and32_4_numbers:This module gets 4 32-bit input and give the answer of and operation of four input.This module use **and32** module 3 times.

or32_8_numbers:This module gets 8 32-bit input and give the answer of or operation of eight input.This module use **or32** module 7 times.

full_adder:This module gets two 1-bit input and give the answer of add operation of two input.

_4bit_adder:This module gets two 4-bit input and give the answer of add operation of two input.This module use **full_adder** module 4 times.

_32bit_adder:This module gets two 32-bit input and give the answer of add operation of two input.This module use **_4bit_adder** module 8 times.

_32bit_subtractor:This module gets two 32-bit input and give the answer of subtract operation of two input.This module gets negative of second number using **xor32** module and **_32bit_adder** module.After that,it add two numbers.

slt_32:This module gets two 32-bit input and give the answer of set less than operation of two input.This module subtract second input from first input using **_32bit_subtractor**.Than,it decide that's operation using most significant bit of subtraction operation.

[illegible]